

# Application Note AN 4110

## Charger Control IC for Off-Line Lithium-Ion Battery Charger

### 1. Charger characteristics of Lithium-Ion Battery

Required characteristics for charging Lithium-ion

battery are constant voltage and constant current control. Curves in Fig 1 show the basic charging characteristics for Li-ion battery in terms of time variation.

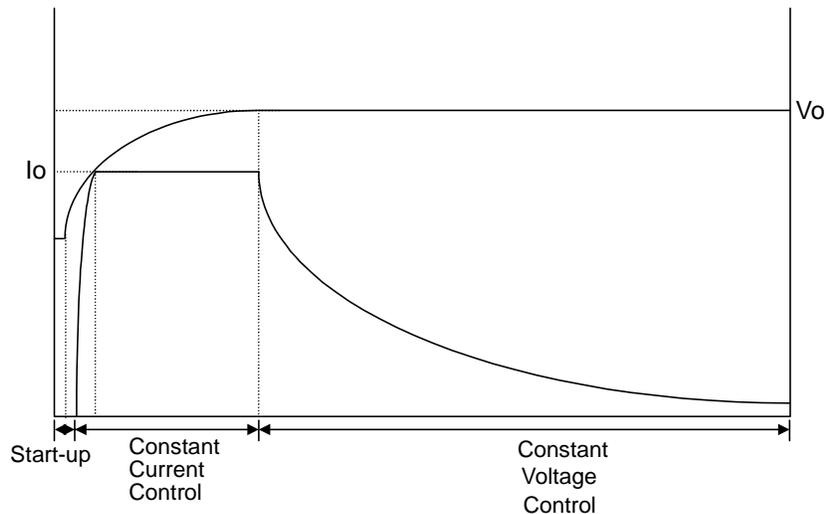


Figure 1. Lithium - Ion Charger

### 2. Functions of FAN7563/4

FAN7563 (FAN7564) was carefully designed to achieve the required characteristics as follows. FAN7563 has basically three functions, which are voltage sensing for constant voltage, peak charging(load) current sensing for constant current and

a charging current monitoring function for the charging state. In addition to these functions of FAN7563, FAN7564 has a LDO driving circuitry with an output sensing terminal and a detection function to guarantee the proper voltage level for an external micro controller.

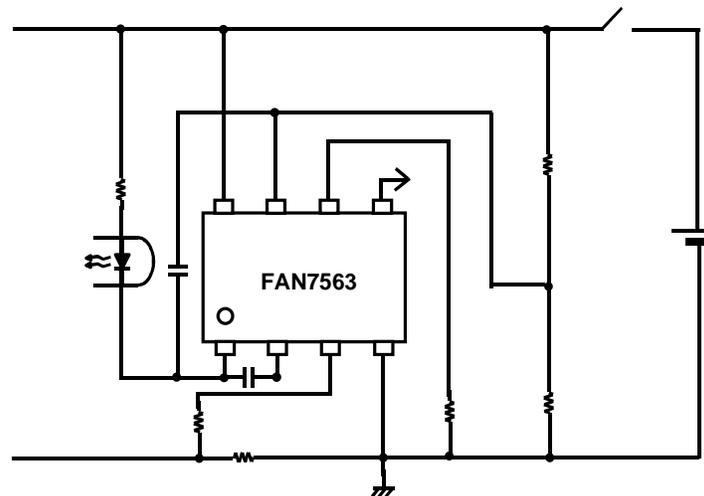


Figure 2. Typical application circuit of FAN7563



addition to the functions of FAN7563.

1. It has a LDO driving circuitry for supply voltage to micro controller.
2. It senses the charging state of battery with external resistors.
3. It senses the supply voltage level of the micro controller.

the micro controller caused by getting out the range of the supply voltage of the micro controller, which means that, with this function, the micro controller can operate within the adequate supply voltage range. Fig. 4. shows the internal blocks of FAN7564 except the same function blocks of FAN7563.

Vr

pin #8 (LDO driving output) provides the supply voltage to the micro-controller with an external PNP transistor, an electrolytic capacitor and three resistors. Pin #9 (ERR) is to sense the condition of supply voltage of micro controller to avoid malfunctioning of

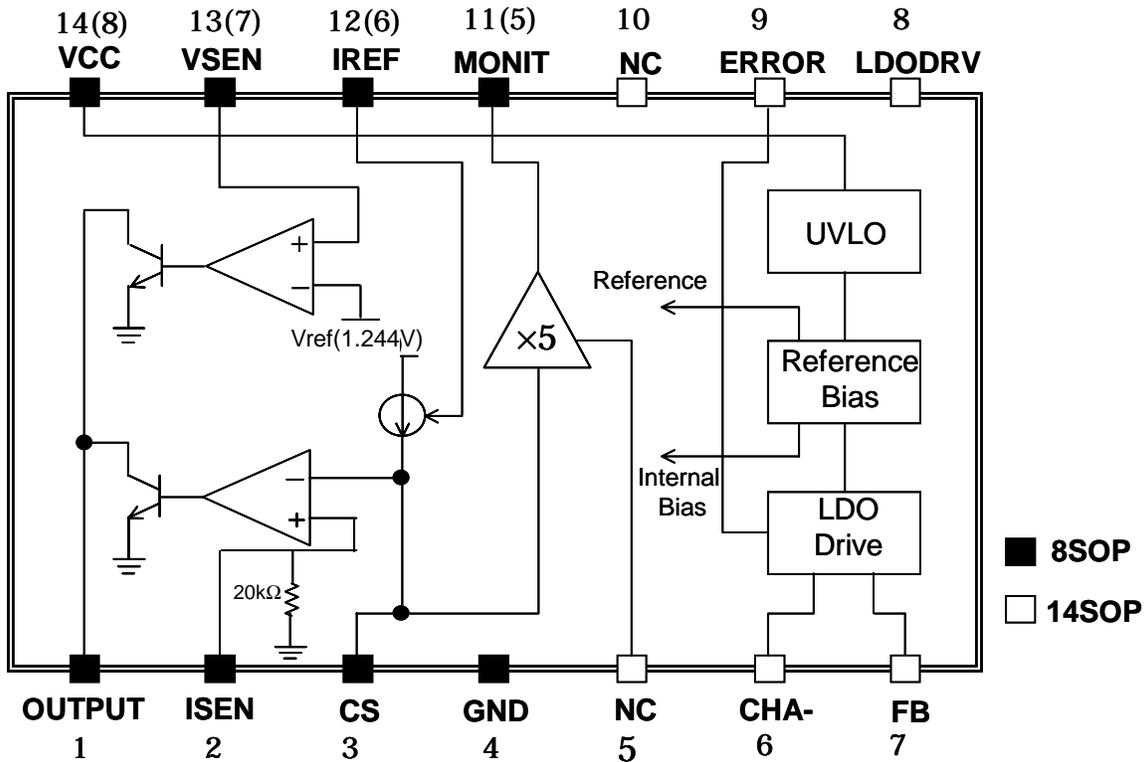


Figure 4. FAN7564 block diagram

Pin # 11 (Moni) has an amplified voltage level, which is five times in comparison with CS voltage level, derived from pin # 3 (CS) of FAN7563, and this voltage level will be used to sense the charging state in the micro controller. Additionally, we can obtain a suitable amplifying ratio in the internal multiplier (x5) if R1 and R2 are properly set.