

The current through the LEDs is held stable by current source  $T_5$ . It is essential for good thermal stability that the transistors and associated diodes ( $T_3$  and  $D_1$ , and  $T_4$  and  $D_2$ ) are mounted in close contact.


Before the mains is switched on, set  $P_1$  to maximum resistance. Switch on the mains, wait for about a minute and then adjust  $P_1$  for a quiescent current through  $T_{10}$  and  $T_{11}$  of 15 mA, corresponding to a voltage drop of 150 mV across  $R_{23}$  and  $R_{24}$ .

Since the amplifier is d.c. coupled throughout, the likelihood of a fairly high direct voltage at the output would be great, the more so because the input transistors are not truly complementary. This is, however, obviated by an active d.c. correction that holds the direct voltage at the output at zero in all circumstances. For this purpose, the output signal is passed via low-pass filter  $R_{26}$ - $C_{13}$  to integrator IC<sub>1</sub>. This arrangement does not affect fast variations of the signal. If, however, the output signal has a d.c. component,  $T_{12}$  will con-

duct to some degree, so that the bases of  $T_1$  and  $T_2$  are pulled into a negative direction. In a negative direction, because  $T_1$  (n-p-n) has an inherently greater voltage amplification ( $\times 3$ ) than  $T_2$  (p-n-p).

Adjust  $P_2$  immediately on switch-on for as low a direct voltage at the output as possible. From then on, any variations caused by temperature changes will be corrected by  $IC_1$ . The speed at which the correction takes place can be increased by giving  $R_{26}$  and  $R_{27}$  lower values.

It is important for optimum

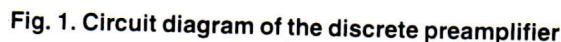

(measured with an output of 1 V r.m.s. across 47 k $\Omega$ )

ELEKTOR ELECTRONICS JULY/AUGUST