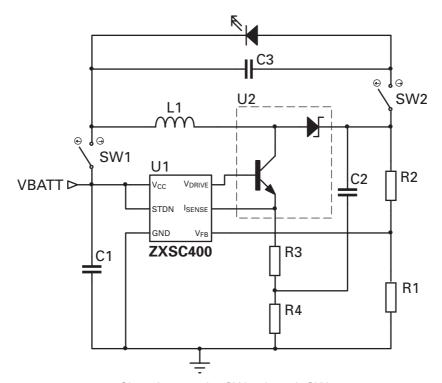


# DN74 ZXSC400 Photoflash LED reference design

#### **Description**

This design note shows the ZXSC400 driving a Photoflash LED. The input voltage is 3V with a maximum pulsed output current of 1A for 2ms.

A typical schematic diagram is shown in Figure 1.



Charging mode: SW1 closed, SW2 open Discharging mode: SW1 open, SW2 closed

Figure 1 Schematic diagram

#### Operation

In charging mode, SW1 is closed and SW2 is open the ZXSC400 is configured as a typical boost converter, charging capacitor C2 up the regulated output voltage set by the ratio of R1 and R2. This is typically 16V. The peak current of the converter (current drawn from the battery) is controlled by R3 plus R4, and is typically 280mA for this application. When C2 is charged to 16V the SW1 is opened and SW2 is closed, converting the ZXSC400 to a step down converter to provide a 1A constant current for 2ms to the photoflash LED. During step down operation, current flows from C2, through the photoflash LED, L1, U2 and is returned to C2 through R3. This means that the peak current is set at a higher value than in charging mode, typically 1A. When the current reaches it's peak value, U2 is switched off and current flows from L1 through the Schottky diode in U2, to the photoflash LED. This cyclic process is repeated until C2 is discharged.

## **DN74**

| Ref | Value         | Part number  | Manufacturer | Comments              |
|-----|---------------|--------------|--------------|-----------------------|
| U1  |               | ZXSC400E6    | Zetex        | LED Driver in SOT23-6 |
| U2  |               | ZX3CDBS1M832 | Zetex        | Dual NPN and Schottky |
| L1  | 12μΗ          | Generic      | Generic      | I <sub>SAT</sub> =1A  |
| R1  | 10kΩ          | Generic      | Generic      | 0805 size             |
| R2  | 510k $\Omega$ | Generic      | Generic      | 0805 size             |
| R3  | 22m $\Omega$  | Generic      | Generic      | 0805 size             |
| R4  | 100m $\Omega$ | Generic      | Generic      | 0805 size             |
| C1  | 1μF           | Generic      | Generic      |                       |
| C2  | 150μF         | Generic      | Generic      |                       |
| C3  | 1μF           | Generic      | Generic      |                       |

Table 1 Bill of materials

2

### **Typical operating waveforms**

(For typical application circuit where  $V_{BATT} = 3V$  and  $T_{amb} = 25^{\circ}C$  unless otherwise stated)

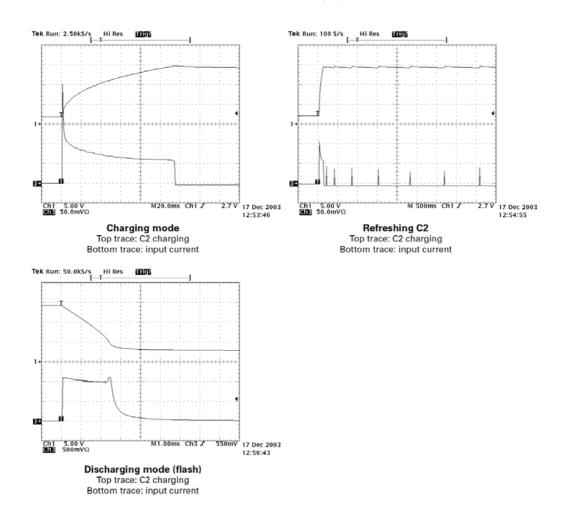


Figure 2 Performance graphs

**DN74** 

Intentionally left blank

Europe Zetex GmbH Streitfeldstraße 19 D-81673 München Germany

Telefon: (49) 89 45 49 49 0 Fax: (49) 89 45 49 49 49 europe.sales@zetex.com Americas

Zetex Inc 700 Veterans Memorial Highway Hauppauge, NY 11788

,,,,

Telephone: (1) 631 360 2222 Fax: (1) 631 360 8222 usa.sales@zetex.com **Asia Pacific** 

Zetex (Asia Ltd) 3701-04 Metroplaza Tower 1 Hing Fong Road, Kwai Fong Hong Kong

Telephone: (852) 26100 611 Fax: (852) 24250 494 asia.sales@zetex.com **Corporate Headquarters** 

Zetex Semiconductors plc Zetex Technology Park, Chadderton Oldham, OL9 9LL United Kingdom

Telephone: (44) 161 622 4444 Fax: (44) 161 622 4446 hq@zetex.com

For international sales offices visit www.zetex.com/offices

Zetex products are distributed worldwide. For details, see www.zetex.com/salesnetwork

This publication is issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contact or be regarded as a representation relating to the products or services concerned. The company reserves the right to alter without notice the specification, design, price or conditions of supply of any product or service.