

Charging Photo-Flash Capacitors Using the TPS65552A

*Sahana Chandra**PMP Portable Power*

ABSTRACT

The TPS6555x family of devices are highly integrated flyback converters used to charge photo-flash capacitors. This document contains a reference design and an example of a PCB design using the TPS65552A.

1 Features

- Highly Integrated Solution to Reduce Components
- Integrated 50-V Power Switch,
 $R_{(ON)} = 200\text{ m}\Omega$ Typical
- Integrated IGBT Driver
- High Efficiency
- Programmable Peak Current, 0.95 A ~ 1.8 A
- Input Voltage of 1.8 V to 12 V
- Optimized Control Loop for Fast Charge Time
- Sensing All Trigger From Primary Side
- 10-Pin MSOP/16-Pin QFN Package
- Protection
 - MAX On Time
 - Over V_{DS} Shutdown
 - Thermal Monitor

2 TPS65552A Reference Design

The Texas Instruments TPS6555xEVM-097 evaluation module (EVM) helps designers evaluate the operation and performance of the TPS6555x family of devices. These devices are highly integrated flyback converters used to charge photo-flash capacitors.

The reference design in Figure 1 contains one fully functional photo-flash charger capable of charging a photo-flash capacitor to 300 V from a battery with voltage between 1.8 V and 12 V. It also provides a flash lamp and trigger circuit to help evaluate charging characteristics.

3 Schematic and Bill of Materials

This section provides the TPS6555xEVM-097 schematic (see [Figure 1](#)) and bill of materials.

3.1 Schematic

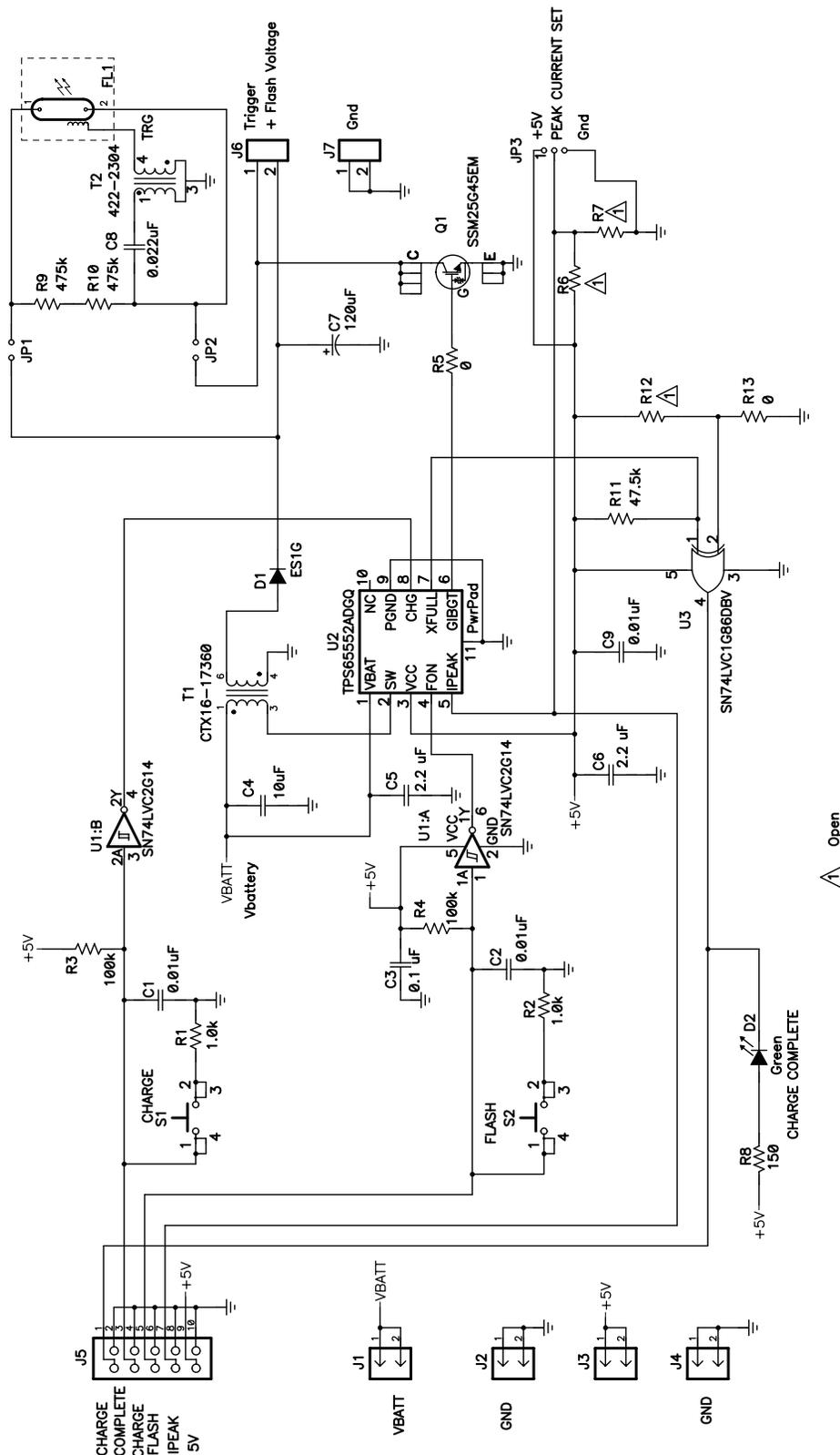


Figure 1. TPS6555xEVM-097 Schematic

3.2 Bill of Materials

Table 3.3. TPS6555xEVM-097 Bill of Materials

COUNT	Ref Des	DESCRIPTION	SIZE	MFR	PART NUMBER
3	C1, C2, C9	Capacitor, Ceramic, 0.01-uF, 50-V, X7R, 10%	0603	TDK	C1608X7R1H103KT
1	C3	Capacitor, Ceramic, 0.1-uF, 50-V, X7R, 10%	0603	TDK	C1608X7R1H104K
1	C4	Capacitor, Ceramic, 10-uF, 16-V, X7R, 10%	1206	TDK	C3216X7R1C106KT
2	C5, C6	Capacitor, Ceramic, 2.2-uF, 16-V, X7R, 10%	0805	TDK	C2012X7R1C225KT
1	C7	Capacitor, Aluminum, 120-uF, 330-VDC, ±20%	13 x 28 mm	Rubycon	330 FW 120A
1	C8	Capacitor, Ceramic, 0.022-uF, 630-V, X7R, 10%	1206	TDK	C3216X7R2J223KT
1	D1	Diode, Rectifier, 1-A, 400-V	SMA	Diodes Inc.	ES1G
1	D2	Diode, LED, Green, Gullwing, GW Type, 20ma, 7.5 mcd typ.	0.120 x 0.087	Panasonic	LN1361CTR
1	FL1	Flash Tube, 400v Max	2.126 x 0.157	Xicon	36FT050
4	J1 - J4	Header, 2-pin, 100mil spacing, (36-pin strip)	0.100 x 2	Sullins	PTC36SAAN
1	J5	Header, 2x5-pin, 100mil spacing (36-pin strip)	0.100 x 5 X 2	Sullins	PTC36SAAN
2	J6, J7	Terminal Block, 2-pin, 15-A, 5.1mm	0.40 x 0.35	OST	ED1609
2	JP1, JP2	Header, 2-pin, 100mil spacing, (36-pin strip)	0.100 x 2	Sullins	PTC36SAAN
1	JP3	Header, 3-pin, 100mil spacing, (36-pin strip)	0.100 x 3	Sullins	PTC36SAAN
1	Q1	Trans, NChan Insulated-Gate Bipolar, 450V, 150A	SO-8	Silicon Standard	SSM25G45EM
1	R1, R2	Resistor, Chip, 1.0k-Ohms, 1/16-W, 1%	0603	Std	Std
1	R11	Resistor, Chip, 47.5k-Ohms, 1/16-W, 1%	0603	Std	Std
2	R3, R4	Resistor, Chip, 100k-Ohms, 1/16-W, 1%	0603	Std	Std
2	R5, R13	Resistor, Chip, 0-Ohms, 1/16-W, 5%	0603	Std	Std
0	R6, R7, R12	Resistor, Chip, xx-Ohms, 1/16-W, 1%	0603		
1	R8	Resistor, Chip, 150-Ohms, 1/16-W, 1%	0603	Std	Std
2	R9, R10	Resistor, Chip, 475k-Ohms, 1/8W, 1%	1206	Std	Std
2	S1, S2	Switch, SPST, PB Momentary, Sealed Washable	0.245 X 0.251	C & K	KT11P2JM
1	T1	Transformer, Flyback, 1:10.2	0.300 x 0.240	Coiltronics	CTX16-17360
1	T2	Transformer, Trigger	0.197 Dia	Xicon	422-2304
1	U1	IC, Dual Schmitt-Trigger Inverter	SOT23-6	TI	SN74LVC2G14DBV
1	U2	IC, Photo Flash Charger and IGBT Driver	DGQ10	TI	TPS65552ADGQ
1	U3	Single 2-Input X-OR Gate	SOT-25	TI	SN74LVC1G86DBV
1	--	PCB, 4.4 In x 4.2 In x 0.062 In		Any	HPA097
3	--	Shunt, 100-mil, Black	0.100	3M	929950-00
4	--	Bumpon, Transparent	0.44" x 0.2"	3M	SJ5303

4 PCB Design With the TPS65552A

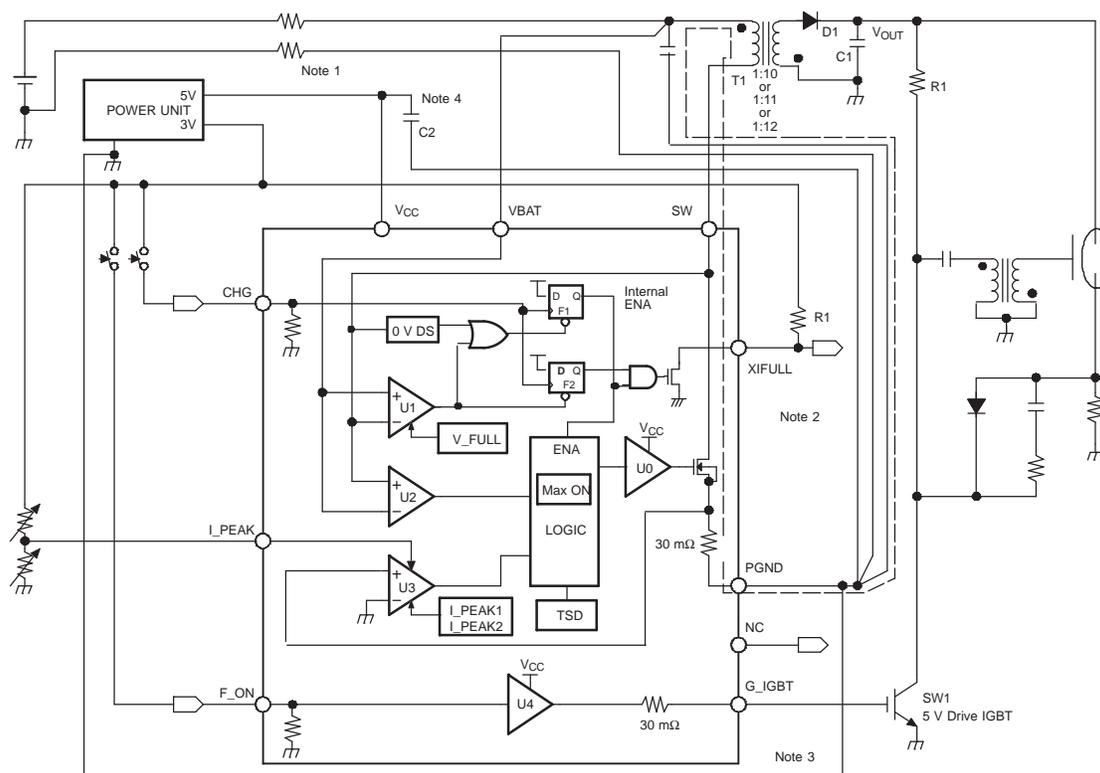


Figure 2. PCB Design Guideline

4.1 Advantages to the TPS65552A

1. These devices can be designed into a smaller area, and require few external components because of the integrated IGBT driver.
2. The peak current on the primary-side inductor can be set to a maximum of 1.8 A by external voltage reference. This makes it possible to control battery life, to protect against system shutdown by large currents, and to change the charging time.
3. By selecting the proper external components, it is possible to achieve 70% or greater efficiency and charging time less than 4 seconds with a battery voltage of 4.2 V and the voltage on the I_PEAK pin more than 1.4 V.

To maximize TPS65552A performance:

1. Choose a diode with the best T_{rr} speed, and select a transformer with the best coefficient of coupling. These affect charging time and efficiency.
2. Good system layout of the PCB can result in enhanced performance.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
Low Power Wireless	www.ti.com/lpw	Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265

Copyright © 2006, Texas Instruments Incorporated