



220VAC>

K30N60 pinout



Modelling indicates motor current range of 0 to 24A gives an output (IV) voltage range of 0 - 3.2V (Motor rated 0–10.5A)

Similarly, MV ranges 0- 3.6V for voltage range of 0 - 200V (Motor rated for 180V)

Note for a DC motor speed (rpm) is proportional to supply voltage and current is proportional to motor torque

Motor control and protection:

Power turned on, charges caps through R55.

SMPS controller starts providing power to PIC and treadmill user control panel

HV voltage increases to 3.6V as caps charge (ie to -320V DC or caps fully charged)

PIC allows RLA2 to close through PIC pin 10

User clicks power switch which causes RLA2 to close its contacts and PIC reads this through PIC pin 9

PIC starts motor PWM based on user selected speed, measures RPM, HV, IV and MV.

If MV > 180V - trip motor (excess voltage ie speed)

If MV < 0V - trip motor as motor is generating

If HV > 3.6V - trip motor as excessive input voltage

If HV < 3.6V - trip motor as excessive current being drawn or something wrong with the incoming supply

If IV > 2V then motor overloaded as motor current > 10.5A
IV may exceed 2V to 3.2V (24A) for brief periods — say when a large user steps onto the treadmill belt so IV should have a 1s or so time delay before it trips the motor If the treadmill belt is heavily loaded the PWM duty cycle is high, then the user suddely steps off, the motor will speed up instantly, so IV suddenly falls but the RPM rises quickly

So HV and IV are analog inputs and MV can be analog or an interrupt

RPM is not sensed by an interrupt capable pin, but it is an input to a comparator on the PIc. The comparitor generates an interrupt on match, and is used to count the pulses

LTspice model indicates (resistive load)
IV rises with rising load current — 2V @10ohm, 1.3V @ 30ohm
MV rises decreasing load current — 4.5V @ 30ohm, 2.8V @ 10ohm
HV rises with increasing load current — 4.2V @ 10ohm, 2V @ 10ohm

Not guaranteed to be correct — use at your own risk Reverse engineered by Happymacer



File: copy redrawn pf906 dc motor driver board.kicad_sch Title: PF906 treadmill DC power schematic

The state of the s		
Size: A3	Date: 2022-12-27	Rev: 3a
KiCad E.D.A. ki	cad (6.0.10)	ld: 1/8

Approx +13VDC @ no load Vbias U3 L78L05 470u 25V +5V +5V +5V + C14 C13 + C12 470u 25V RH1 10D-9 **R13** 10M Approx
-14VDC
-Vbias
L79L05 1N4007 **D3** 150 1W 15n R39 D9 C41 VS2KBB or similar V_display_power Neutral **R14** 47u 50V C11 + 47u 50V + C10 Measures at 14V, @ no load C33___ D4 GND2 U5 TL431LP


Auxiliary power schematic


Not guaranteed to be correct — use at your own risk Reverse engineered by Happymacer



Sheet: /2 Aux power/
File: Aux power.kicad_sch

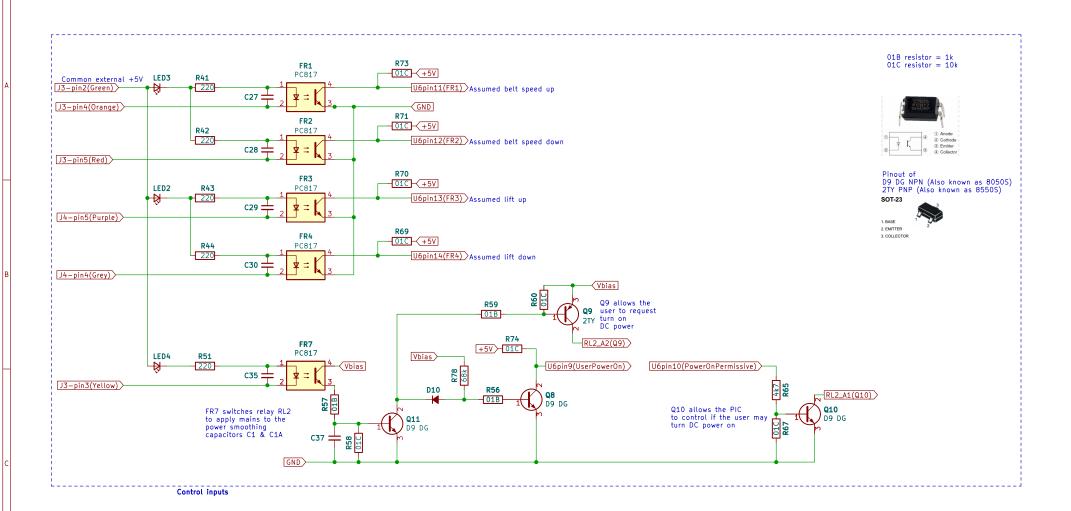Title: PF906 treadmill DC power schematic
Size: A3 Date: 2022-12-27
KiCad E.D.A. kicad (6.0.10) **Rev: 3a** Id: 2/8



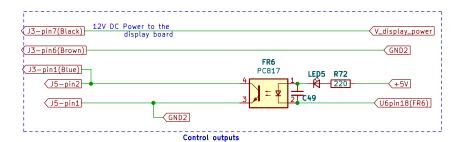

Colours on connectors match cable colours and colors on the display board

Control input/output schematic

Not guaranteed to be correct — use at your own risk Reverse engineered by Happymacer




Sheet: /3 Control IO/ File: Control IO.kicad_sch


Title: PF906 treadmill DC power schematic

 Size: A3
 Date: 2022–12–27
 Rev: 3a

 KiCad E.D.A. kicad (6.0.10)
 Id: 3/8



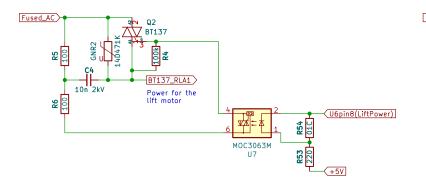

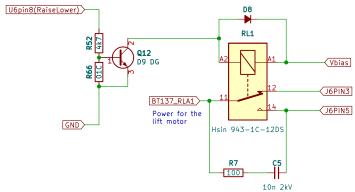

Lift motor power schematic


Not guaranteed to be correct — use at your own risk Reverse engineered by Happymacer

Sheet: /4 Lift Motor Control/ File: Lift Motor Control.kicad_sch

Title: PF906 treadmill DC power schematic

Size: A3 Date: 2022-12-27 KiCad E.D.A. kicad (6.0.10) **Rev: 3a** Id: 4/8

RPM sensor

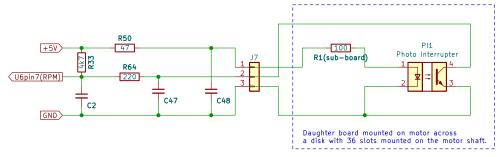

Max motor speed is 4700RPM so max pulse rate is 4700*36/60 = 2820Hz

So considering PWM frequency, it may be best to use a PWM frequency >> 2820Hz so say 30kHz. Im not sure if thats relevent,

RPM is not sensed by an interrupt capable pin, however it does connect to the inverting input of either Comparator 1 or Comparator 2 of the PIC chip. Either comparator can generate an internal interrupt.

Consider that when a hole in the disk moves to expose the LED. As the hole approaches the light level increases, reaches a peak then drops again. Much like a a typical day, where the sun rises at dawn and sets at dusk but its niot an abrupt light level change. Pushing the light signal through a compartor therefore makes sense to square off the wave and trigger on the rising or falling edges of the wave.

Counting the pulses from this wave is thus simplified by using a comparator and its interrupt in the PIC.

Motor RPM sensor

Not guaranteed to be correct — use at your own risk Reverse engineered by Happymacer

Happymacer

Sheet: /5 RPM / File: RPM.kicad_sch

Title: PF906 treadmill DC power schematic

 Size: A3
 Date: 2022-12-27
 Rev: 3a

 KiCad E.D.A. kicad (6.0.10)
 Id: 5/8

+5V (pin2) SC1IN+/ICSPDAT/ULPWU/ANO/RAO
19
C12IN0-/ICSPCLK/Vref/AN1/RA1
C10UT/TOCKI/INT/AN2/RA2
Vpp/MCLR/RA3
T1G/OSC2/CLKOUT/AN3/RA4
T1CKI/OSC1/CLKIN/RA5
2 RCO/AN4/C2IN+ RC1/AN5/C12IN1-RC2/AN6/C12IN2-/P1D RC3/AN7/C12IN3-/P1C RC4/C20UT/P1B RC5/CCP1/P1A RC6/AN8/SS Assumed lift down U6pin14(FR4)
U6pin7(RPM) +5V R68 1k U6pin8(RaiseLower)
U6pin2(TotemControl) (U6pin5(PWM_out)) (U6pin8(LiftPower)) (U6pin9(UserPowerOn)) SDI/SDA/AN10/RB4 1: RX/DT/AN11/RB5 1: SCK/SCL/RB6 1: TX/CK/RB7 1: U6pin13(FR3) Assumed lift up
U6pin12(FR2) Assumed belt speed down
U6pin11(FR1) Assumed belt speed up
U6pin10(PowerOnPermissive) C7/AN9/SDO +5V R61 PIC16F690-ISS R61 may interfere with PWM of the Arduino GND ICSP_GND(pin3)

PIC 16F690 controller schematic

Not guaranteed to be correct — use at your own risk Reverse engineered by Happymacer




Sheet: /6 PIC 16F690 Controller/ File: PIC 16F690 Controller.kicad_sch

Title: PF906 treadmill DC power schematic

Size: A3 Date: 2022-12-27 KiCad E.D.A. kicad (6.0.10)

Rev: 3a

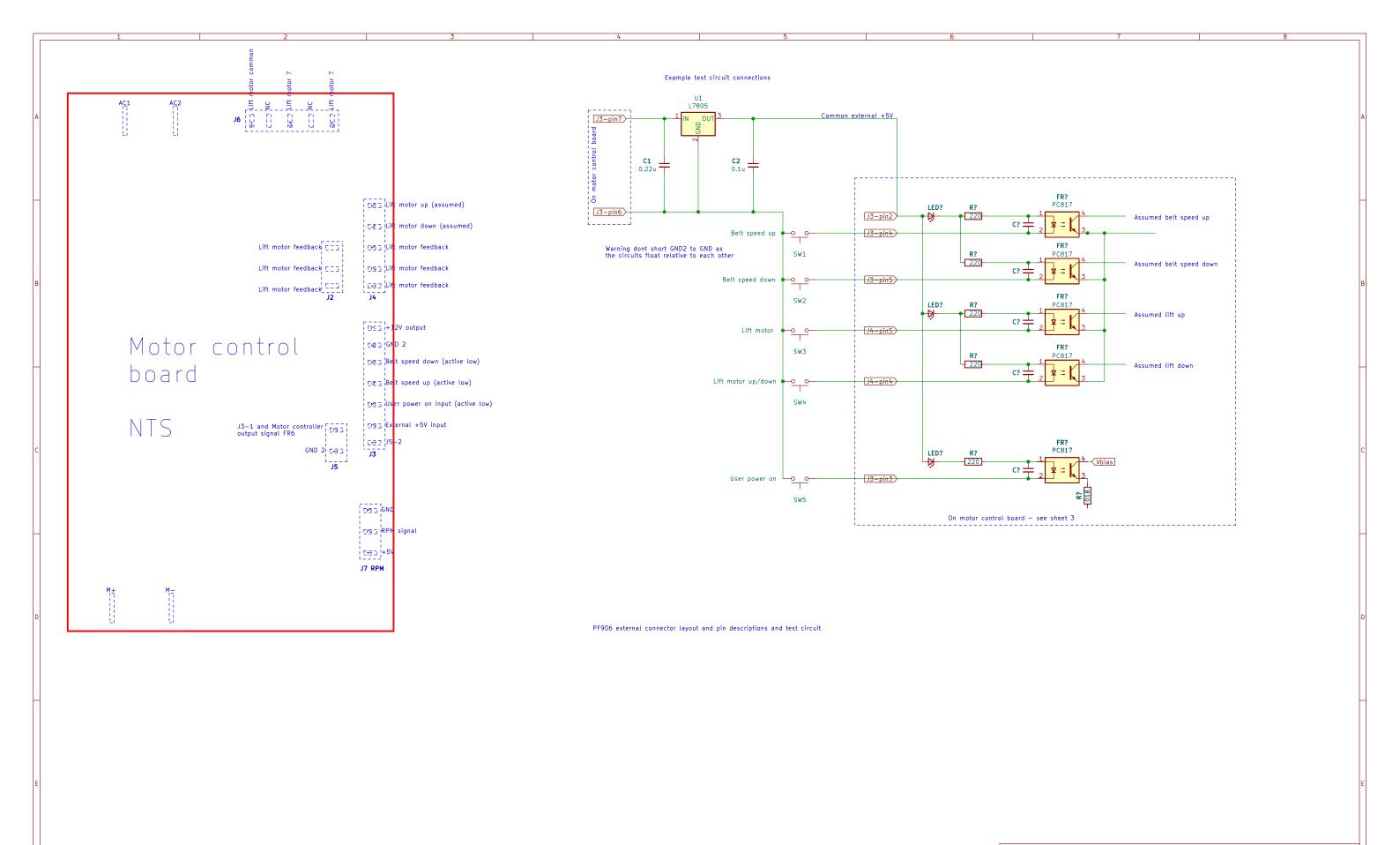

Not guaranteed to be correct — use at your own risk
Reverse engineered by Happymacer

Sheet: /7 Connector layout/
File: conn_layout.kicad_sch

Title: PF906 treadmill DC power schematic

Size: A3 Date: 2022-12-27 Rev: 3a

KiCad E.D.A. kicad (6.0.10)

